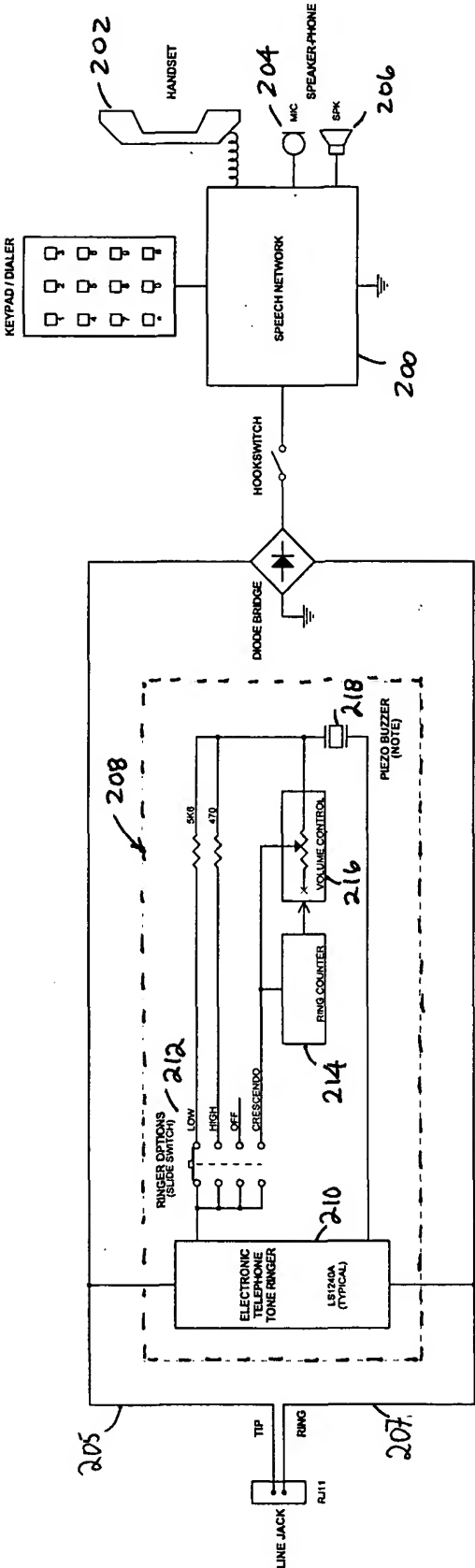


FIGURE 1

20

CRESCENDO RINGER CIRCUIT
OPERATED DIRECTLY FROM LINE (TIP & RING)



NOTE: PIEZO BUZZER CAN BE REPLACED WITH A SPEAKER

FIGURE 2